



SoulShift - Educational Q&A Platform

General Questions

Practice Questions



Q1. What is the purpose of an operational amplifier?

- A. To rectify AC signals
- B. To amplify voltage signals
- C. To switch electronic signals
- D. To store charge

Solution: Operational amplifiers are designed to amplify voltage signals, often used in various analog applications.



